

# CS981: Advanced Topics On Cryptography

Name: Mohammed Jawed

StudentID: 93356 00 19

<u>Q.</u>	<u>Page NO.</u>
(i)	2
(ii)	3
(iii)	4
(iv)	5 - 7
(v) <u>Part 1</u>	8 - 9
<u>Part 2</u>	10 - 12

CS981


Assignment 5

Mohammed Jameel

Student ID - 233560019

- ① controlled controlled NOT gate is also called as "Toffoli Gate".

using Basic quantum Gates.

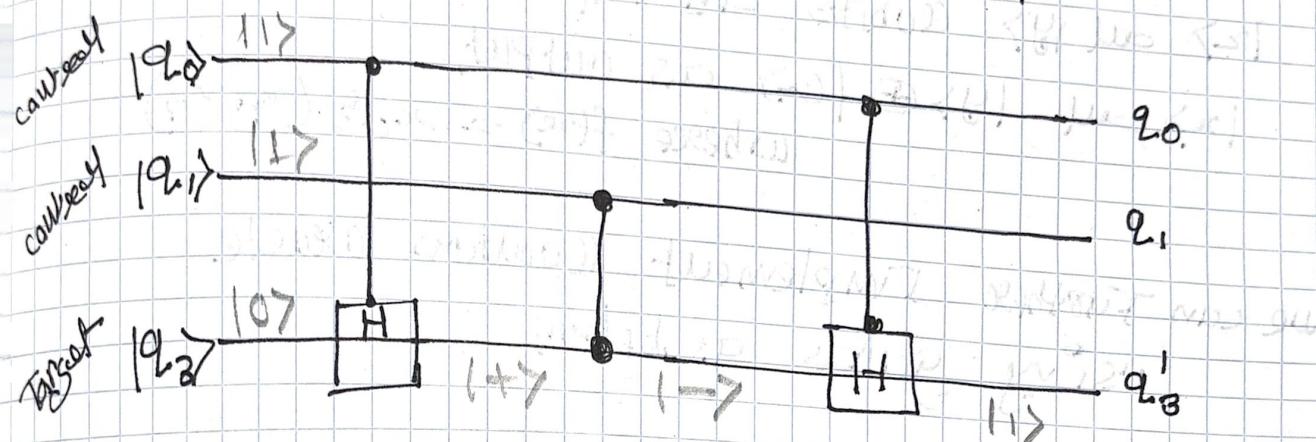


CCNOT gate is type of CNOT gate with two control qubits and one Target qubit ( $|q_3\rangle$ ).

The target qubit ( $|q_3\rangle$ ) will be inverted if the first ( $|q_0\rangle$ ) and second ( $|q_1\rangle$ ) qubits are both 1.

Truth Table


I/P			O/P			target
$q_0$	$q_1$	$q_2$	$q_0$	$q_1$	$q_2$	
0	0	0	0	0	0	
0	0	1	0	0	1	
0	1	0	0	1	0	
0	1	1	0	1	1	
1	0	0	1	0	0	
1	0	1	1	1	1	
1	1	0	1	1	1	
1	1	1	1	1	0	

target  
controlled flip (inverted)

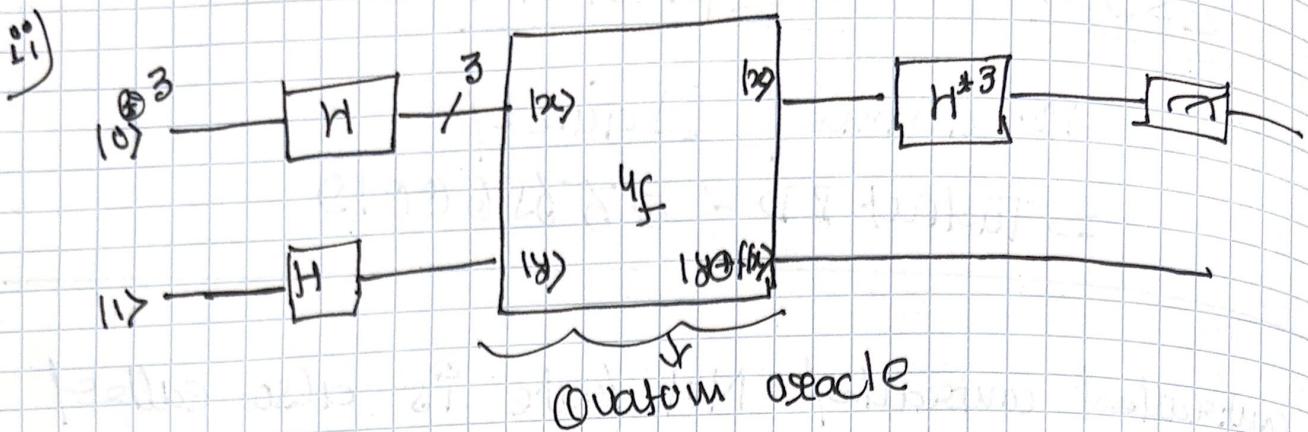

the above black box (Quantum oracle) will takes  
 |x> and |y> qubits as input and produces  
 |x> and |y>  $\oplus f(x)$  as output,  
 where  $f(x) = x_0 \oplus (x_1 \cdot x_2)$

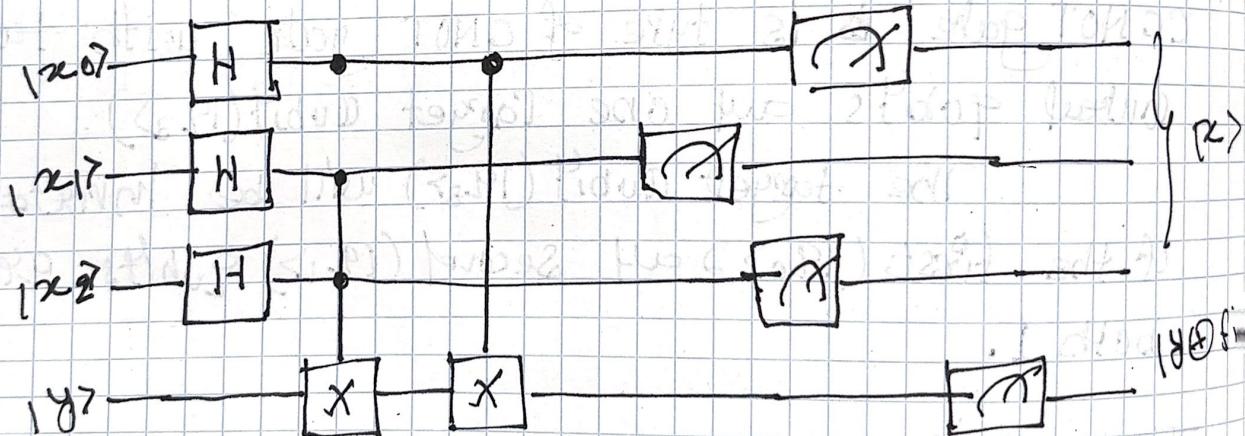we can further implement Quantum oracle  
 using gates as below,



- 1)  $x_0, x_1, x_2$  are in superposition. Using Hadamard gates.  
 → this will testing all combination in 1 execution
- 2) The X gate compute  $(x_1, x_2)$  and stores the result in qubit y.
- 3) A CNOT gate compute  $x_0 \oplus (x_1 \cdot x_2)$ , finalizing  $f(x)$  in qubit y.

iii) To comment whether function  $f(x) = x_0 \oplus x_1 \cdot x_2$  is balanced or constant.

- A function  $f(x)$  (boolean) is balanced if it returns 0's for exactly half of all inputs and 1's for the other half.
- On other hand if the boolean function  $f(x)$  is constant function then returns all 0's or all 1's for any input.

Now, let's analyze the function  $f(x) = x_0 \oplus x_1 \cdot x_2$  behaviour to comment,

$$f(x) = x_0 \oplus x_1 \cdot x_2$$


We will use truth-table to analyze it.

for 3 i/p qubits ( $x_0, x_1, x_2$ ), total  $2^3 = 8$  possible I/P combination.

$x_0$	$x_1$	$x_2$	$x_1 \cdot x_2$	$f(x) = x_0 \oplus x_1 \cdot x_2$
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	0

As we can observe from above truth-table o/p ( $f(x)$ ) has 4 0's and 4 1's  
 therefore, boolean function  $f(x)$  is balanced  
 as it produces an equal number of 0s and 1s  
 for all possible I/P combination.

#### iv) Quantum circuit diagrams

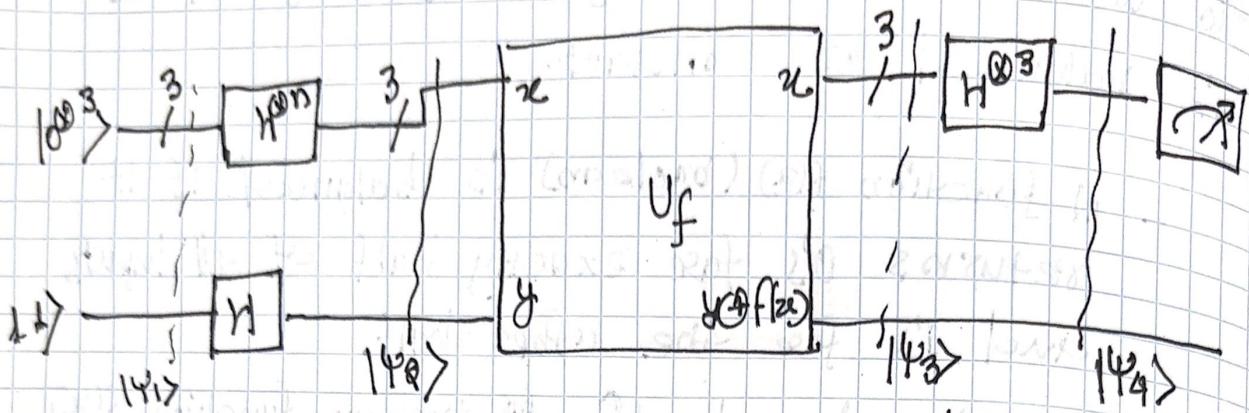

We can use Deutsch-Jozsa Algorithm, to efficiently detect whether provided function is balanced or constant by leveraging quantum superposition and interference.

Above drawn Quantum circuit can detect for balanced or constant.

Let's justify my claim,

as we know,  $f(x) = x_0 + x_1 \cdot x_2$ .

Here,  $n = 3$ .

$x$	$f(x)$
0 0 0	0
0 0 1	0
0 1 0	0
0 1 1	1
1 0 0	1
1 0 1	1
1 1 0	1
1 1 1	0

From Generalize formula, find o/p,

$$|\Psi_4\rangle = \frac{1}{\sqrt{2^n}} \sum_{x \in \{0,1\}^n} \sum_{y \in \{0,1\}^n} (-1)^{f(x)+x \cdot y} |\Psi\rangle$$

where  $n=3$

one from truth table and stated in Q. iii) the function  $f(x)$  is balanced.  
It means,

$\sum_{x \in \{0,1\}^n} (-1)^{f(x)} = 0$ , then we will  
reverse measure  $|0\rangle^{\oplus 3}$ .

Balanceed  
 $M \neq 10^3$

# Solution of Algorithm

$$① |\Psi_1\rangle = |0\rangle^{\otimes 3} |1\rangle$$

Apply a Hadamard gate to each qubits:

$$② |\Psi_2\rangle = \frac{1}{\sqrt{2^4}} \sum_{x=0}^{2^3-1} |x\rangle (|0\rangle - |1\rangle)$$

③ Apply the quantum oracle  $|x\rangle |y\rangle \rightarrow |x\rangle |y \oplus f(x)\rangle$

$$|\Psi_3\rangle = \frac{1}{\sqrt{2^4}} \sum_{x=0}^{2^3-1} |x\rangle (|f(x)\rangle - |1 \oplus f(x)\rangle)$$

$$= \frac{1}{\sqrt{2^4}} \sum_{x=0}^{2^3-1} (-1)^{f(x)} |x\rangle (|0\rangle - |1\rangle)$$

each  $x, f(x)$  is either 0 or 1

④ At this stage ignored second register.  
Apply a Hadamard gate to each qubit in

first register...

$$|\Psi_4\rangle = \frac{1}{2^3} \sum_{x=0}^{2^3-1} (-1)^{f(x)} \left[ \sum_{y=0}^{2^3-1} (-1)^{x \cdot y} |y\rangle \right]$$

$$= \frac{1}{2^3} \sum_{y=0}^{2^3-1} \left[ \sum_{x=0}^{2^3-1} (-1)^{f(x)} (-1)^{x \cdot y} \right] |y\rangle$$

$$|\Psi_4\rangle = \frac{1}{8} \sum_{y \in \{0,1\}^3} \sum_{x \in \{0,1\}^3} (-1)^{f(x) + x \cdot y} |y\rangle$$

lets check

$$|\Psi_1\rangle = |000\rangle |01\rangle$$

$$|\Psi_2\rangle = H^{\otimes 3} |000\rangle H|10\rangle$$

$$|\Psi_3\rangle = \frac{1}{\sqrt{2}} [ |000\rangle + |001\rangle + |010\rangle + |011\rangle + |100\rangle + |101\rangle + |110\rangle + |111\rangle ] \rightarrow$$

$$|\Psi_3\rangle = U_f |\Psi_2\rangle$$

$$= \frac{1}{2\sqrt{2}} [ |000\rangle + |001\rangle + |010\rangle - |011\rangle - |100\rangle - |101\rangle - |110\rangle + |111\rangle ] \rightarrow$$

$|\Psi_4\rangle$  = Apply Hadamard gate to 1<sup>st</sup> register

$$|\Psi_4\rangle = \frac{1}{2\sqrt{2}} [ H|000\rangle + H|001\rangle + H|010\rangle - H|011\rangle - H|100\rangle - H|101\rangle - H|110\rangle + H|111\rangle ] \rightarrow$$

$$|\Psi_4\rangle = \frac{1}{8} [ 4|100\rangle + 4|101\rangle + 4|110\rangle - 2|111\rangle ] \rightarrow$$

$$|\Psi_4\rangle = (\gamma_0|100\rangle + \frac{1}{2}|101\rangle + \frac{1}{2}|110\rangle - \frac{1}{2}|111\rangle) \rightarrow$$

Now, Sum of probabilities  $\gamma_0 + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = \frac{3}{4}$

This indicate Partially destructive interference.

therefore,

- Destructive interference for the state  $|000\rangle$ ,  
Indicate/consistent with a balanced function.

- and Non-Zero amplitudes for multiple states also indicate a balanced function.



Hence, this quantum circuit for given  $f(x)$   
could be able to indicate for balanced function.

Fun!!! =


$\checkmark)$  ~~get~~  $f(x) = s \cdot x \bmod q$

$$x = 5 \text{ bits}$$

$$\text{and } s = 10101.$$

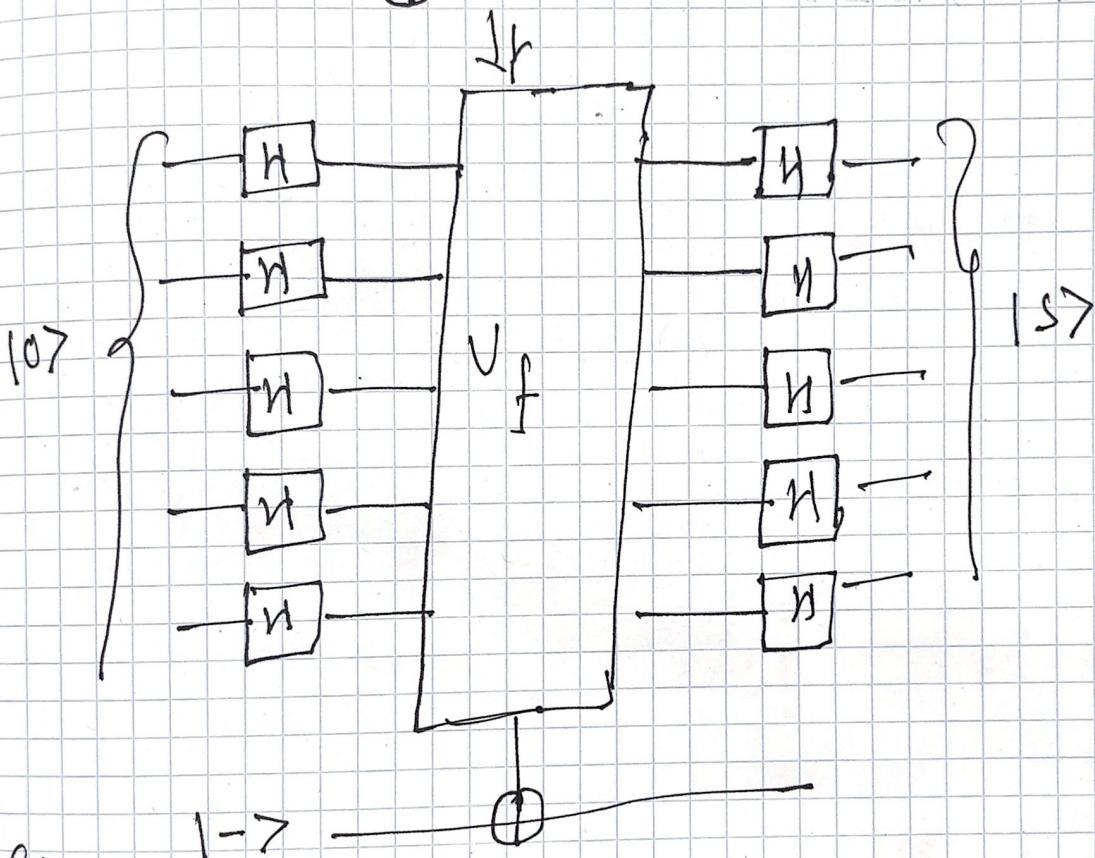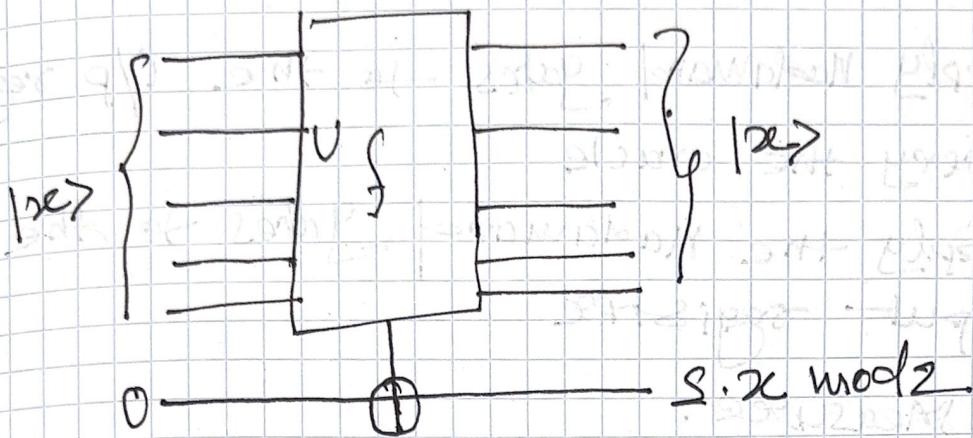

exacte

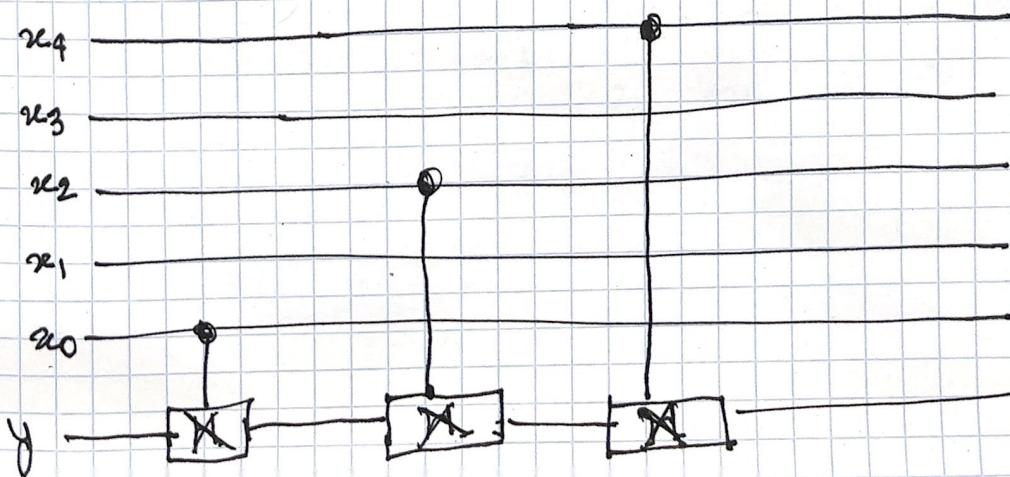


$(y \oplus s \cdot x)$

T-0 -

The Quantum Solution (reference to Part I of Q.V.)

1. Initialize the inputs qubits to the  $|0\rangle^{\otimes 5}$  state, and output qubit to  $|-\rangle$
2. Apply Hadamard gates to the i/p register
3. Query the oracle
4. Apply the Hadamard gates to the input register
5. Measure.

Page - II

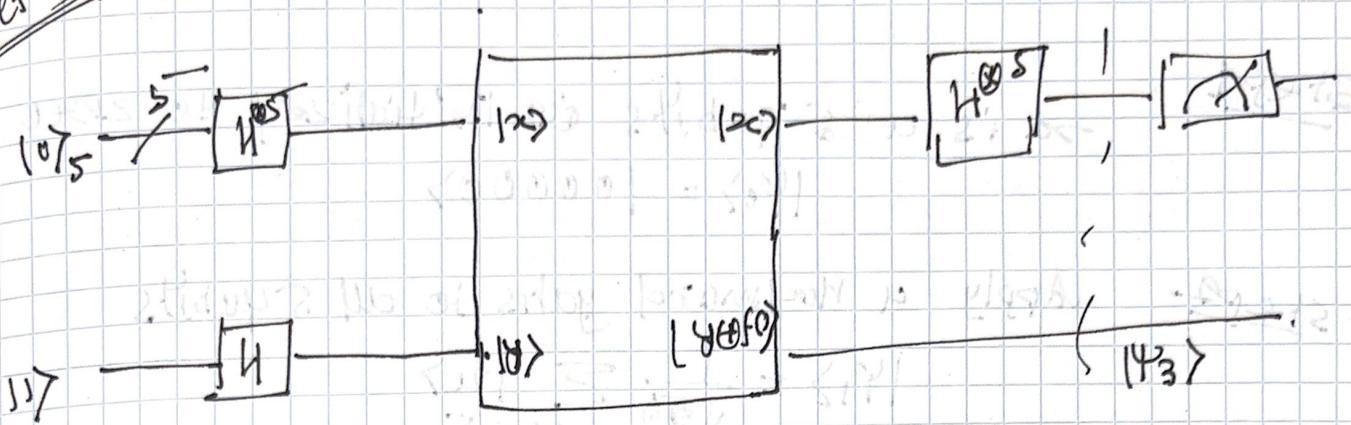

We already know,

$$|\psi_3\rangle = \frac{1}{\sqrt{2^5}} \sum_{(x,y) \in \{0,1\}^5} (-1)^{f(x) + x \cdot y} |y\rangle$$

Let's consider (Measurement) only 1<sup>st</sup> register

$$|\psi_3\rangle = \frac{1}{\sqrt{2^5}} \sum_{x \in \{0,1\}^5} (-1)^{f(x) + x \cdot y}$$

Given,  $f(x) = S \cdot x \bmod 2$ .

$$|\psi_3\rangle = \frac{1}{\sqrt{2^5}} \sum_{x \in \{0,1\}^5} (-1)^{x \cdot S + x \cdot y}$$

$$|\psi_3\rangle = \frac{1}{\sqrt{2^5}} \sum_{x \in \{0,1\}^5} (-1)^{x \cdot (S+y)}$$

This can be written as

$$|\psi_3\rangle = \frac{1}{\sqrt{2^5}} \sum_{j=0}^4 \left[ \sum_{\substack{x \in \{0,1\}^5 \\ x_j=0}} (-1)^{(S_j+y_j)x_j} \right]$$

If  $S=y$  then above value is 1.

If  $S \neq y$ , then there exist  $j$  such that-

$S_j \oplus y_j = 1$ . So the o/p in the case will be 10

So the final o/p will be  $|S101\rangle$ .

Explanation to determine the S value. (wolking)

Step 1

$\rightarrow$  is a 5 qubits initialized to zero

$$|\Psi_0\rangle = |00000\rangle$$

Step 2

Apply a Hadamard gates to all 5 qubits

$$|\Psi_1\rangle = \frac{1}{\sqrt{2}} \sum_{x \in \{0,1\}^5} |x\rangle$$

$$|\Psi_1\rangle = \frac{1}{\sqrt{32}} (|00000\rangle + |00001\rangle + |00010\rangle + \\ + |11111\rangle)$$

Step 3:

Oracle Transformation for  $S = 10101$

the oracle applies the phase  $(-1)^{S \cdot x}$  to each basis state.

$$S \cdot x = s_4 x_4 + s_3 x_3 + s_2 x_2 + s_1 x_1 + s_0 x_0$$

Here,  $s_4 = 1, s_3 = 0, s_2 = 1, s_1 = 0 \neq s_0 = 1$ ,

therefore, the oracle flips the phase of a basis state  $|x\rangle$  if  $x_4 \oplus x_2 \oplus x_0 = 1$

$$|\Psi_2\rangle = \frac{1}{\sqrt{32}} \sum_{x \in \{0,1\}^5} (-1)^{S \cdot x} |x\rangle \quad \left| \begin{array}{l} \text{if } S \cdot x = 0, \text{ phase } + \\ \text{if } S \cdot x = 1, \text{ phase } - \end{array} \right.$$

~~cancel out~~

$$|\Psi_2\rangle = \frac{1}{\sqrt{32}} (|00000\rangle - |00001\rangle - |00010\rangle + |00011\rangle - |00100\rangle \\ + |00101\rangle + |00110\rangle - |00111\rangle + \dots + |11111\rangle)$$

Step 4: Applying Hadamard gate to all qubits.

$$|\Psi_3\rangle = H^{\otimes 5} |\Psi_2\rangle = H^{\otimes 5} \left( \frac{1}{\sqrt{32}} \sum_{x \in \{0,1\}^5} (-1)^{S \cdot x} |x\rangle \right)$$

$$|\Psi_3\rangle = \frac{1}{\sqrt{32}} \sum_{Z \in \{0,1\}^5} (-1)^{S \cdot Z} H^{(0)} |Z\rangle$$

$$H^{(0)} |Z\rangle = \frac{1}{\sqrt{32}} \sum_{Z \in \{0,1\}^5} (-1)^{Z \cdot Z} |Z\rangle$$

Now,  $|\Psi_3\rangle = \frac{1}{\sqrt{32}} \sum_{Z \in \{0,1\}^5} \left( \sum_{X \in \{0,1\}^5} (-1)^{S \cdot Z + X \cdot Z} \right) |Z\rangle$

on simplification,

$$\underline{|\Psi_3\rangle = |S\rangle = |10101\rangle}$$

This in single query the designed quantum circuit is able to give secret  $S = \underline{10101}$